

Training Schedule

Lecture 1: VHDL Introduction

Lecture 2: Concurrent" and Sequential VHDL

Lecture 3: RTL Definition

Lecture 4: Signals and Types


Lecture 5: VHDL Operators

Lecture 6: Synthesis VHDL Coding Styles


Lecture 7: Testbench Coding in VHDL

Lecture 8: Advanced VHDL


VHDL Language

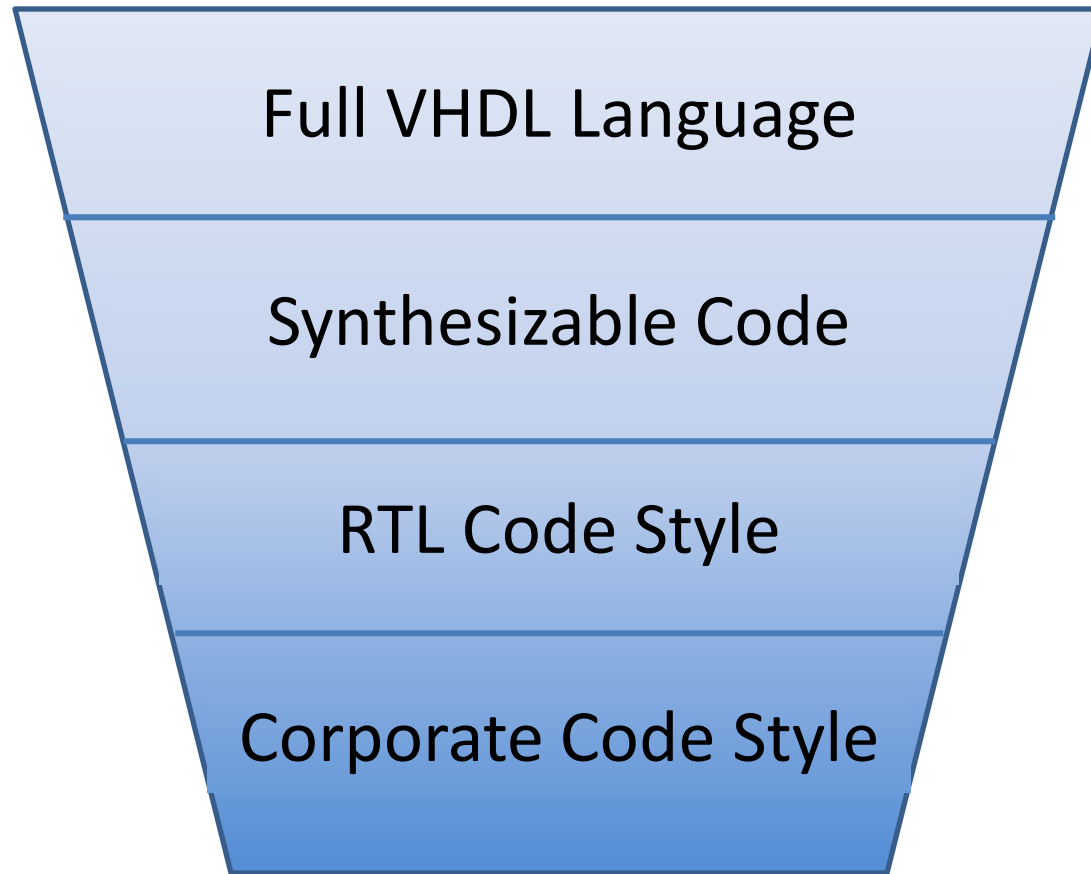

Schematic Design Flow

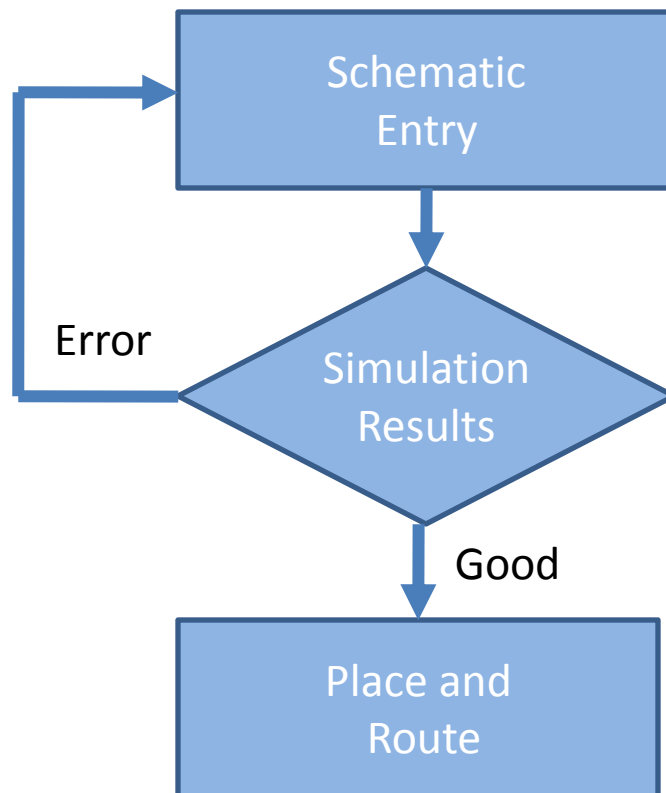


VHDL Design Flow

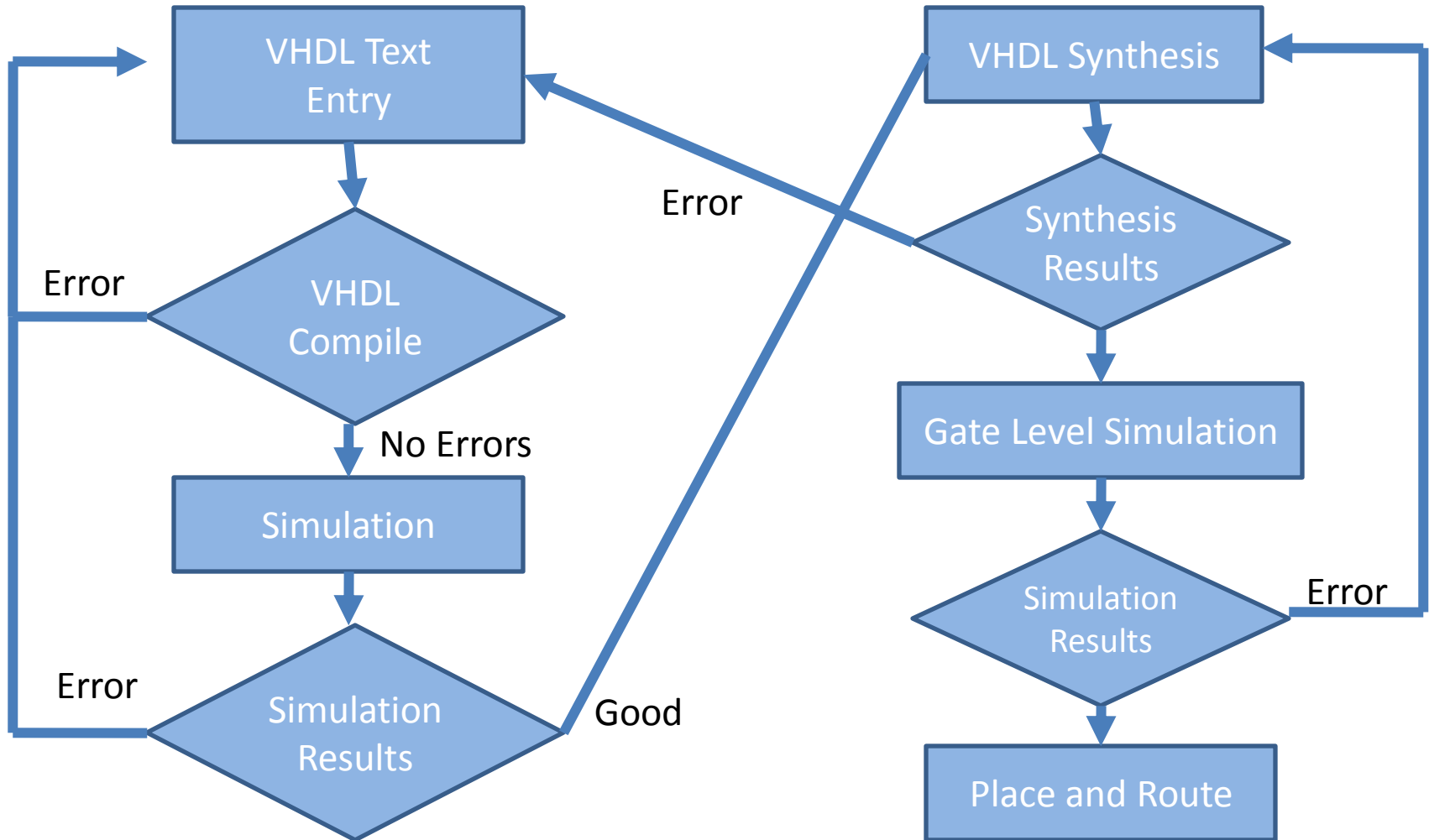

VHDL Structure


VHDL	Schematic
Interface	Symbol
Behavior	Logic
Configuration	Schematic Hierarchy

VHDL Structure (Typical)

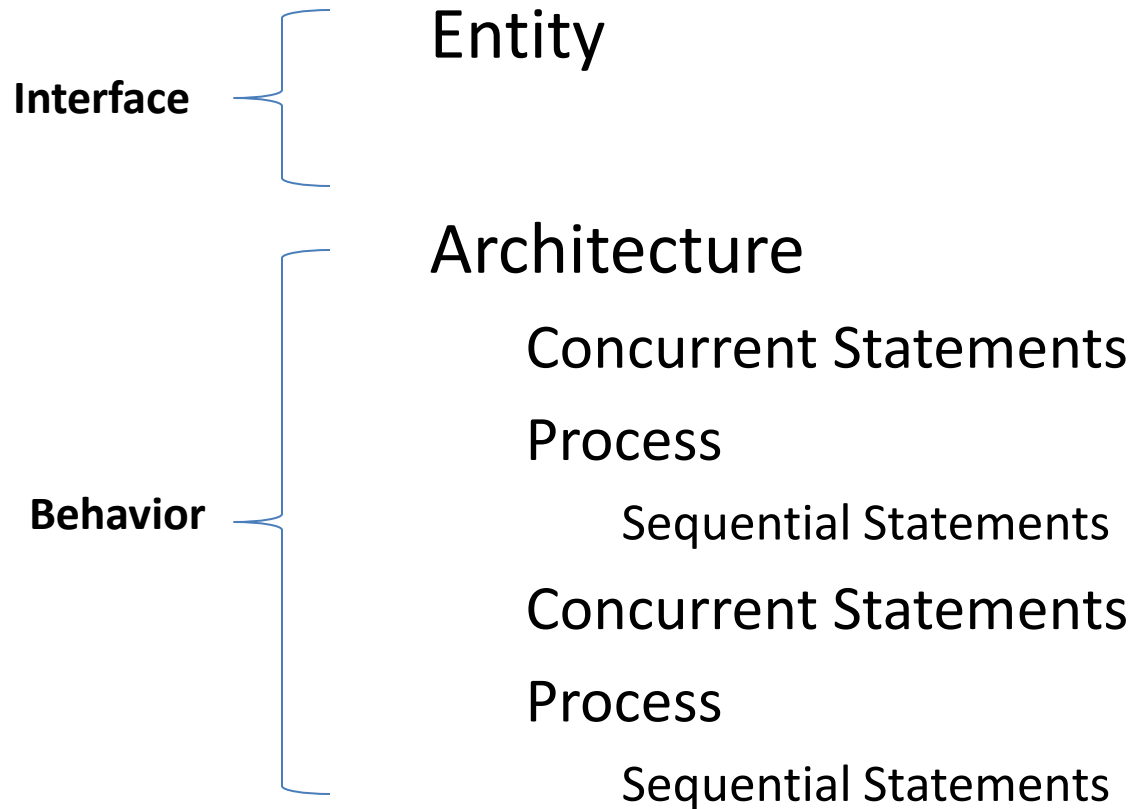

Entity
 
```
entity MUX is  
  port ( A   : in  Std_logic;  
        B   : in  Std_logic;  
        SEL : in  Std_logic;  
        C   : out Std_logic  
        );  
end MUX
```




Entity Syntax

entity identifier **is**
 [port (port interface list);
end [entity] [identifier];

-
- Defines the Interface
 - Is Associated with one or more Architectures

Entity Structure

 


Architecture Syntax


```
architecture identifier of entity-name is  
begin  
  {architecture body}  
end [architecture ] [identifier];
```

- Behavior is defined
- Is Associated with a single Entity


Architecture Structure

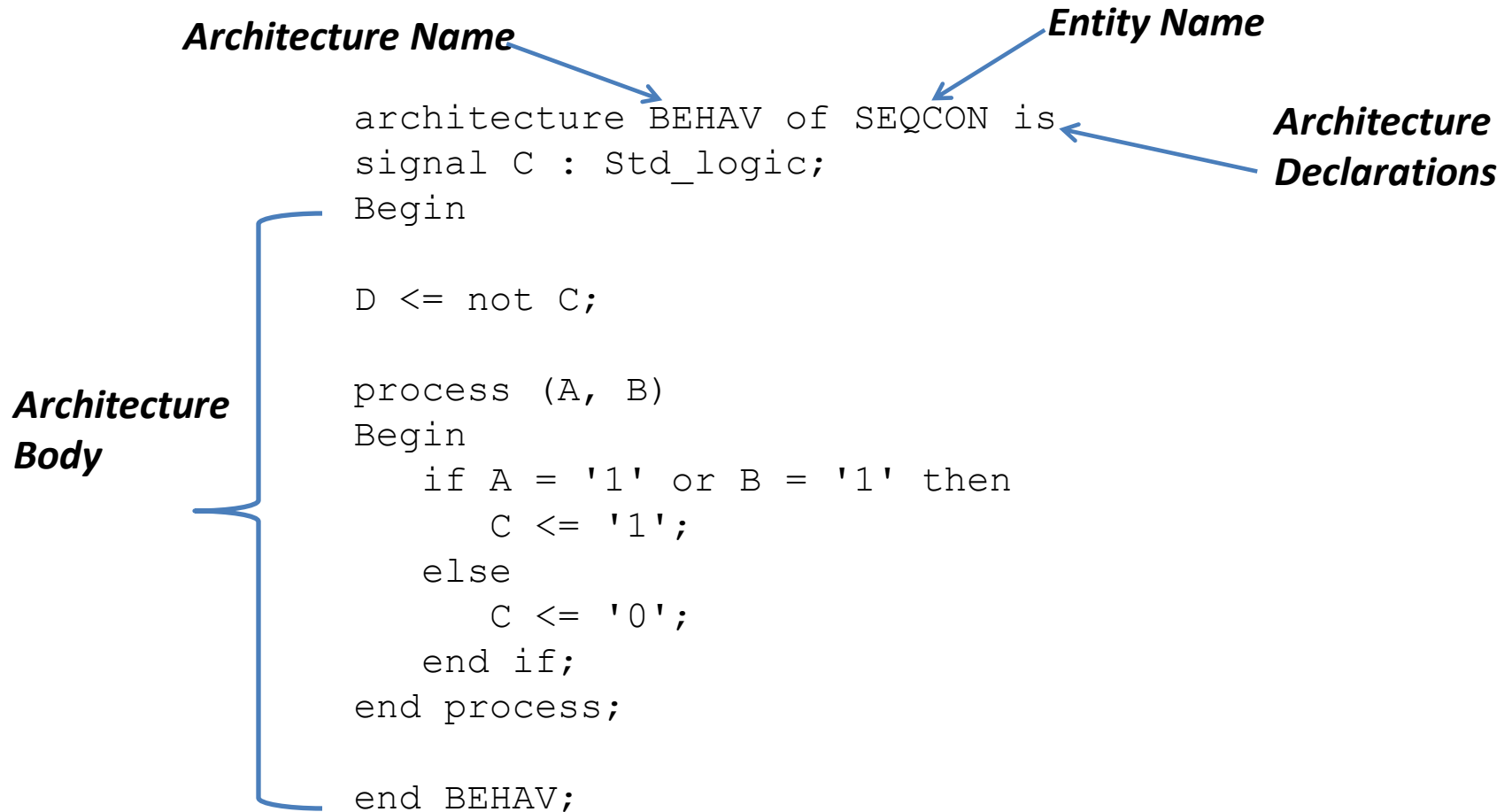

Sequential Definition

 

Flowcharts

 

- Statements executed sequentially
- "Software Model"


Concurrent Definition

Statement #1

Statement #2

Statement #3

Statement #4

 

- Statements executed simultaneously
- “Hardware Model”

Process Syntax

```
process_label: process (signal list)  
begin  
end process [process_label];
```

-
- Contains Only Sequential Statements
 - Executes Concurrently with other Processes

Sequential vs. Concurrent

```
SEQ: process (A, B)
begin
    if A = '1' and B = '1' then
        C<='1';
    else
        C<='0';
    end if;
end process;
```

Sequential

```
C <= (A and B);
```

Concurrent

Process Structure

Process Label

Sensitivity List

**Sequential
Statements**

```
MUX_Proc: process (A,B,SEL)
Begin
    if SEL = '1' then
        C <= A;
    else
        C <= B;
    end if;
end process;
```


Process Characteristics

```
MUX_Proc: process (A,B,SEL)
Begin

    if SEL = '1' then
        C <= A;
    else
        C <= B;
    end if;

end process;
```

What happens when the sensitivity list is incomplete?

Process Rules

- Process executes when signal in sensitivity list changes
- Process contains only sequential statements
- Signal assignments occur at the "end process" statement
- Signals get the last executed assignment

Concurrent Example

```
entity CONEX is
port ( A    : in  Std_logic;
      B    : in  Std_logic;
      C    : out Std_logic);
end CONEX ;

architecture BEHAV of CONEX is
begin

    C <= A or B;

end behav;
```

What behavior does this code represent?

Sequential Example

```
entity SEQEX is
port ( A    : in  Std_logic;
      B    : in  Std_logic;
      C    : out Std_logic);
end SEQEX ;

architecture BEHAV of SEQEX is
begin

process (A, B)
begin
    if A = '1' or B = '1' then
        C <= '1';
    else
        C <= '0';
    end if;

end process;

end behav;
```

What behavior does this code represent?

Concurrent & Sequential Example

```
entity SEQ2EX is
port ( A    : in  Std_logic;
      B    : in  Std_logic;
      D    : out Std_logic );
end SEQ2EX ;

architecture BEHAV of SEQ2EX is
signal C : Std_logic;
begin

D <= not C;

process (A, B)
begin
    if A '1' or B = '1' then
        C <= '1';
    else
        C <= '0';
    end if;
end process;

end behav;
```

How do Concurrent and sequential statements interact?

Concurrent vs. Sequential

```
architecture BEHAV1 of SEQCONA is
```

```
begin
```

```
    Z <= X and Y;
```

```
    Z <= X or Y;
```

```
end BEHAV1;
```

Concurrent

```
architecture BEHAV2 of SEQCONA is
```

```
Begin
```

```
process (X, Y)
```

```
Begin
```

```
    Z <= X and Y;
```

```
    Z <= X or Y;
```

```
end process;
```

```
end BEHAV2;
```

Sequential

Draw a block diagram
for the logic
represented by each
architecture

Signal Types and Sizes

```
entity BADCODE is
port ( X_INT   : in   integer;
      Y_NIB    : in   Std_logic_vector(3 downto 0);
      Z_BYTE   : out  Std_logic_vector(7 downto 0);
end BADCODE;

architecture BEHAV of BADCODE is
Begin

Z_BYTE <= X_INT and Y_NIB;
Z_BYTE <= not Y_NIB;

end BEHAV;
```

Signal Types and Sizes
must match

VHDL Syntax

```
entity TEST is
port ( A : in Std_logic;
      B : in Std_logic;
      D : out Std_logic;
end TEST ;

architecture RTL of ORGATE is
signal C : Std_logic;

begin

D <= not C;

process (A, B)
begin
    if A '1' or B = '1' then
        C <= '1';
    else
        C <= '0';
    end if;
end process;

end behav;
```

VHDL Language
Syntax is very strict

Find the errors in this
code.